

# Bridge circuits

## Table of Contents

Introduction.....	1
Bridge circuit.....	1
Quarter bridge.....	2
Quarter bridge with the instrumentation amplifier.....	4
Linearized quarter bridge.....	7
Exersizes.....	11

Copyright (C) 2022 Miodrag Bolic

This program is free software: you can redistribute it and/or modify it under the terms of the GNU General Public License as published by the Free Software Foundation, either version 3 of the License, or (at your option) any later version. This program is distributed in the hope that it will be useful, but WITHOUT ANY WARRANTY; without even the implied warranty of MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the GNU General Public License for more details <<https://www.gnu.org/licenses/>>.

This code was developed by Miodrag Bolic for the book PERVASIVE CARDIAC AND RESPIRATORY MONITORING DEVICES: <https://github.com/Health-Devices/CARDIAC-RESPIRATORY-MONITORING>

```
% Changing the path from main_folder to a particular chapter
main_path=fileparts(which('Main_Content.mlx'));
if ~isempty(main_path)
    %addpath(append(main_path,'/Chapter2'))
    cd (append(main_path,'/Chapter3/Bridges'))
    addpath(append(main_path,'/Service'))
end
SAVE_FLAG=0; % saving the figures in a file
```


## Introduction

In this notebook, we will introduce the bridge circuit, and show how to connect it to the instrumentation amplifier and how to linearize it.

## Bridge circuit



Bridge circuit is show for the figure below. The outout is shown when the resistor R3 changed its value from in the range of 3%.

## Wheatstone Bridge

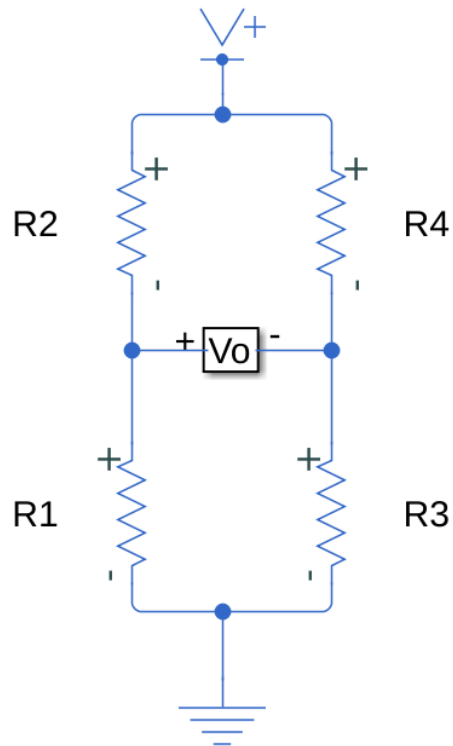

```
% Balanced bridge
model_name = 'bridge1';
open_system(model_name);
set_param('bridge1/R1', 'R', '120');
set_param('bridge1/R2', 'R', '120');
set_param('bridge1/R3', 'R', '120');
set_param('bridge1/R4', 'R', '120');
simOut = sim('bridge1', 'CaptureErrors', 'on');
```

## Quarter bridge

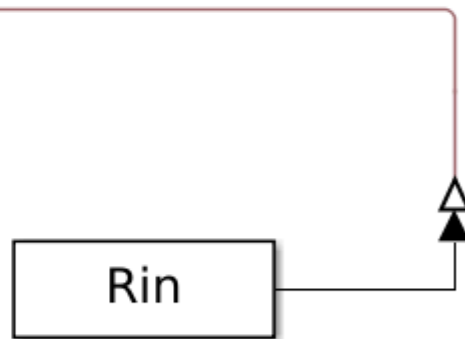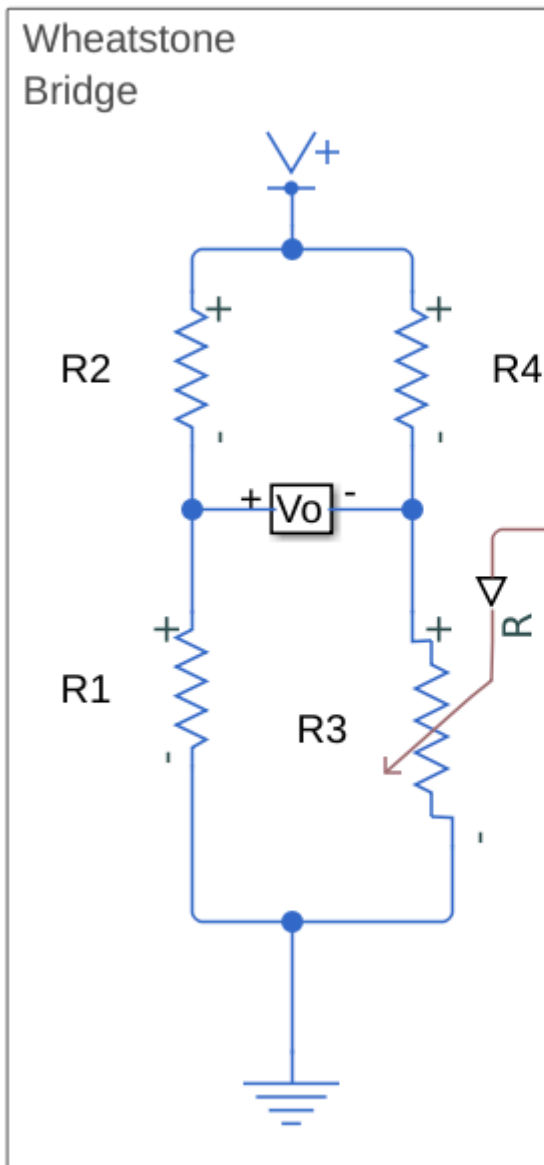

```
% Changing input resistance of R3 over 2 sec from 120Ohm -3% to 120 +3%
T=0.001;
Rin(:,1)=T:T:2; %time;
percentage_change=3;
R_nominal=120;
R_range=[R_nominal-R_nominal*percentage_change/100, R_nominal+R_nominal*percentage_change/100];
deltaR=(R_range(2)-R_range(1))/length(Rin(:,1));
Rin(:,2)=R_range(1):deltaR:R_range(2)-deltaR;
```


```
%Quarter bridge
model_name = 'quarter_bridge';
open_system(model_name);
set_param('quarter_bridge/R1','R','120');
```

```


set_param('quarter_bridge/R2','R','120');
set_param('quarter_bridge/R4','R','120');
simOut1 = sim('quarter_bridge','CaptureErrors','on');

figure
plot(Rin(:,2),simOut1.voltage_out.Data(1:length(Rin(:,2)),1))
title('Response of a quarter bridge')
xlabel('Resistance R3 (Ohm)')
ylabel('Voltage (V)')

```

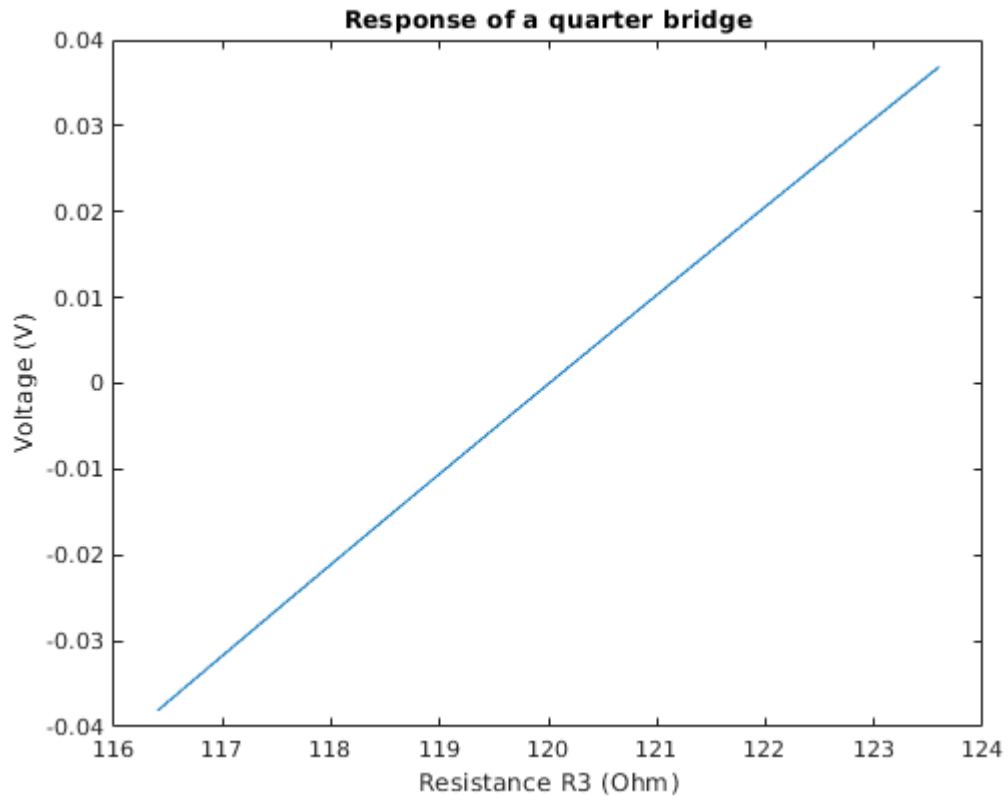
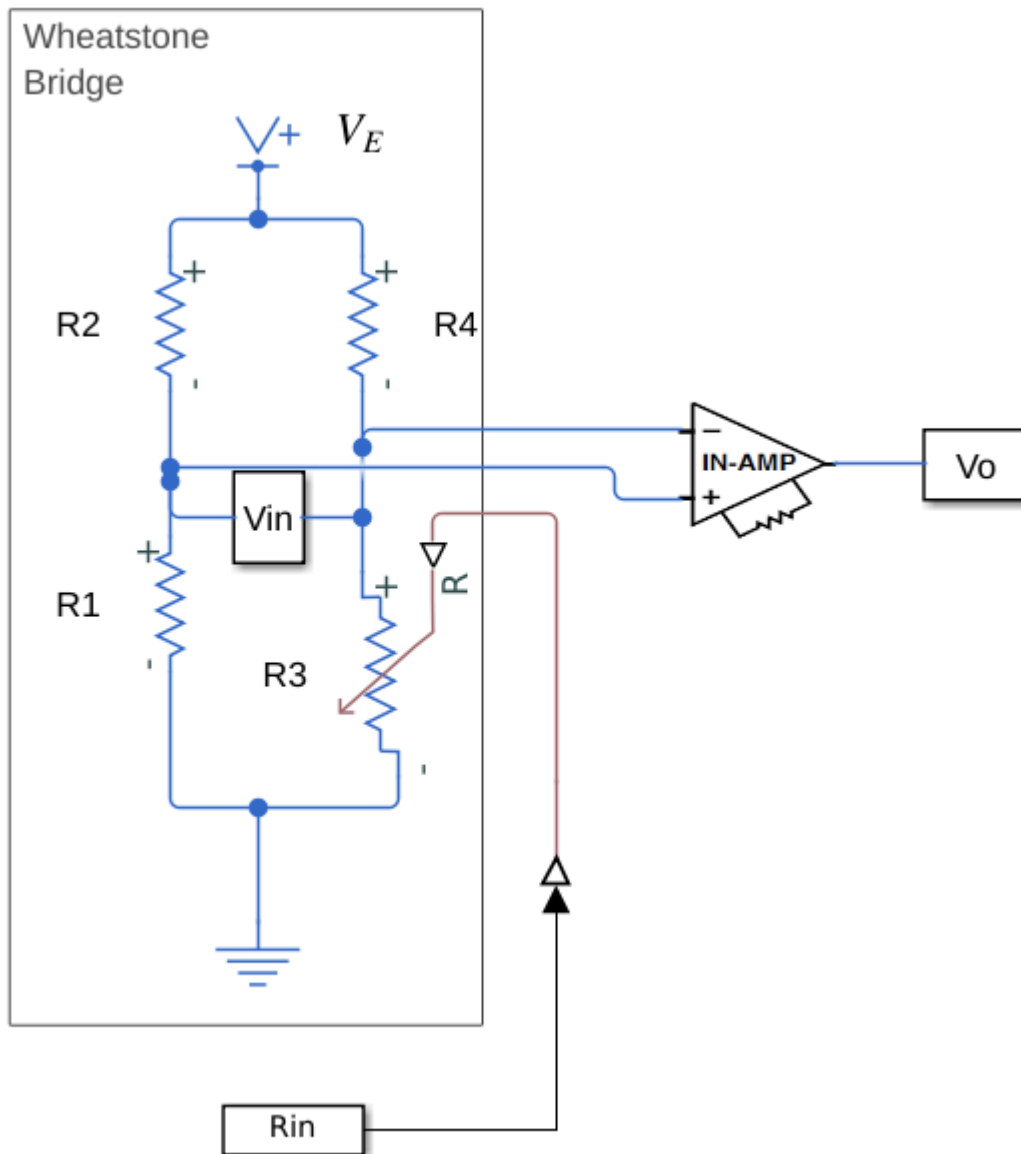
## Quarter bridge with the instrumentation amplifier



```
T=0.001;
t=T:T:2;
Rin(:,1)= t; %time;
percentage_change=3;
R_nominal=120;

Rin(:,2)=R_nominal+sin(2*pi*1.2*t);
```

```
%Quarter bridge
% Get simulation results
model_name = 'quarter_bridge_with_IA';
open_system(model_name);
set_param('quarter_bridge_with_IA/R1', 'R', '120');
```

```

set_param('quarter_bridge_with_IA/R2','R','120');
set_param('quarter_bridge_with_IA/R4','R','120');
out=sim(model_name)

```

```

out =
    Simulink.SimulationOutput:

        ScopeData: [1x1 struct]
        logstdout: [1x1 Simulink.SimulationData.Dataset]
        simout: [1x1 timeseries]
        tout: [6126x1 double]

    SimulationMetadata: [1x1 Simulink.SimulationMetadata]
    ErrorMessage: [0x0 char]


```

```


temp_vin = out.simout.Data(:,1);
temp_vout = out.simout.Data(:,2);

% Plot results
figure
plot(out.simout.Time,temp_vin,'LineWidth',1);
hold on
plot(out.simout.Time,temp_vout,'LineWidth',1);
hold off
grid on
title('Input and output of the amplifier');
ylabel('Voltage (V)');
xlabel('Time (s)');
xlim([0,2])
legend({'Potential difference accross the bridge','Output'});
annonation_save('b',"Fig3.7b.jpg", SAVE_FLAG);

```

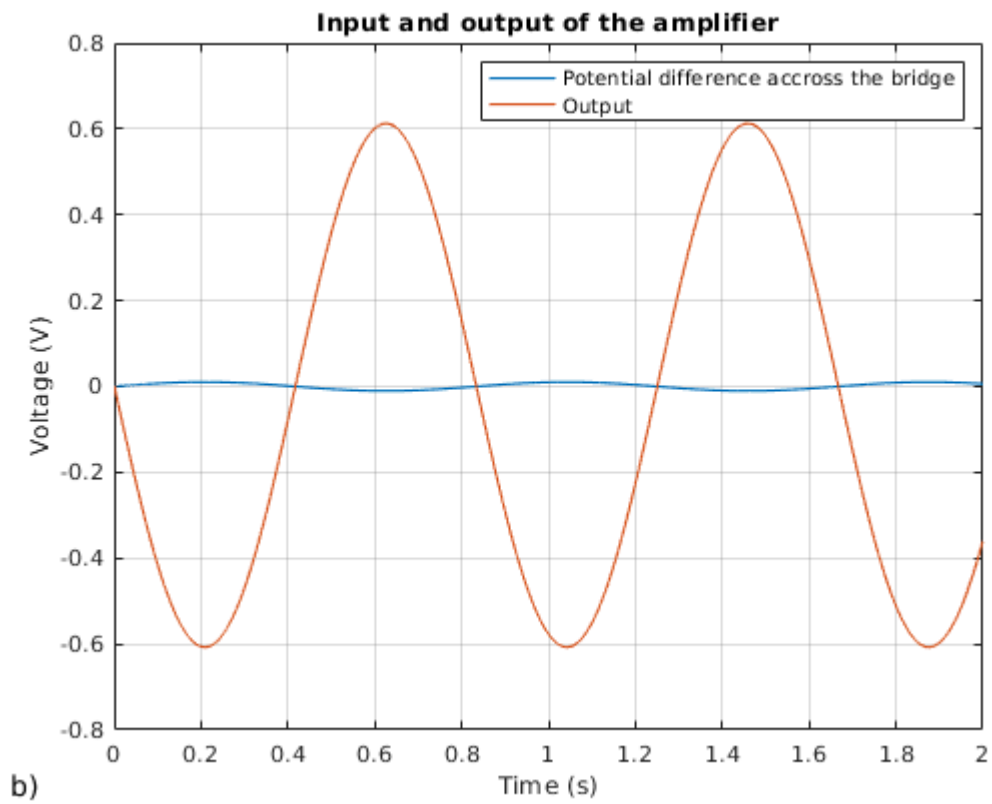

## Linearized quarter bridge

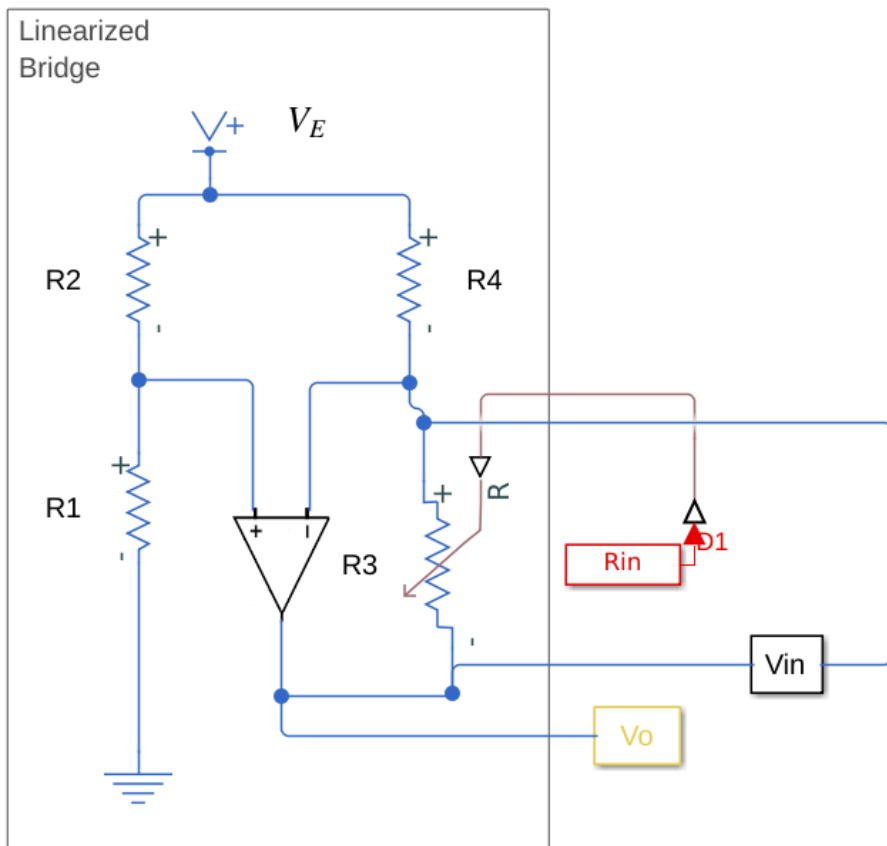

```
% Changing input resistance of R3 over 2 sec from 120ohm -3% to 120 +3%
T=0.001;
t=T:T:2;
Rin(:,1)=T:T:2; %time;
percentage_change=3;
R_nominal=120;

Rin(:,2)=R_nominal+sin(2*pi*1.2*t);
```

```
model_name = 'LinearizedBridge';
out=sim(model_name)
```

```
out =
  Simulink.SimulationOutput:

    ScopeData: [1x1 struct]
    logouts: [1x1 Simulink.SimulationData.Dataset]
    simout: [1x1 timeseries]
    tout: [5932x1 double]

    SimulationMetadata: [1x1 Simulink.SimulationMetadata]
    ErrorMessage: [0x0 char]
```


```
temp_vin = out.simout.Data(:,1);
temp_vout = out.simout.Data(:,2);
```




```

% Plot results
figure
%plot(out.simout.Time,temp_vin,'LineWidth',1);
%hold on
plot(out.simout.Time,temp_vout,'LineWidth',1);
hold off
grid on
title('Output of the bridge');
ylabel('Voltage (V)');
xlabel('Time (s)');
xlim([0.1,2])
annnotation_save('a','Fig3.9a.jpg', SAVE_FLAG);

```

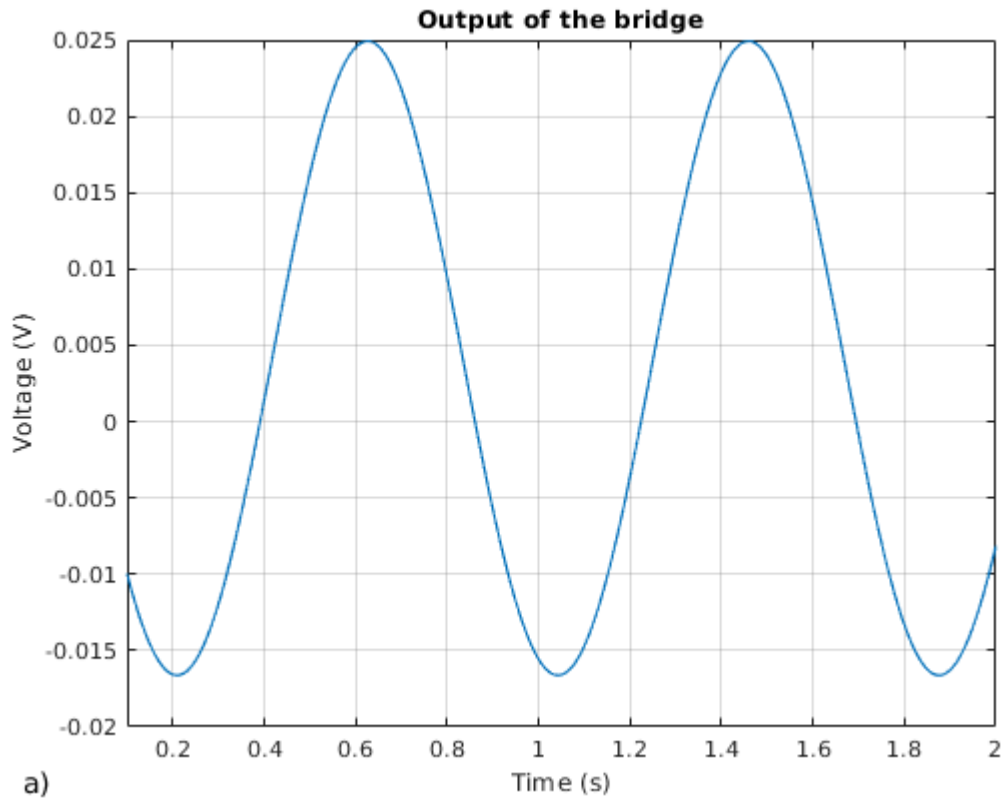

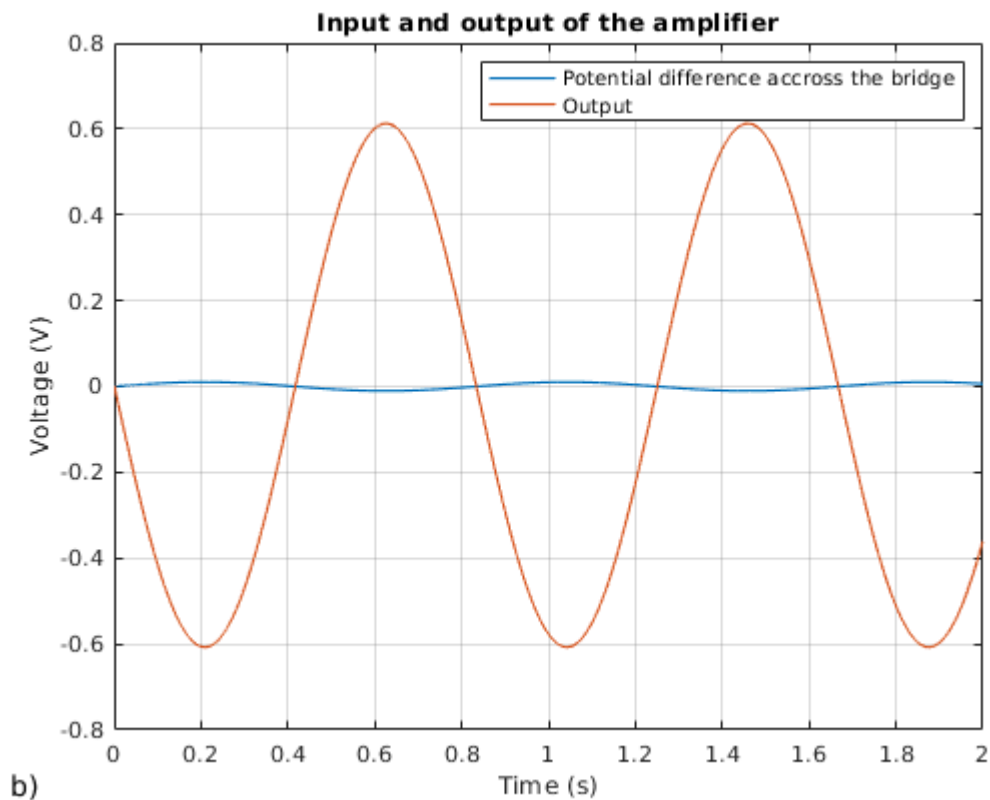

```
%ylim([-0.1,0.1])
%legend({'Voltage over the bridge','Output'});

R_range=[R_nominal-R_nominal*percentage_change/100, R_nominal+R_nominal*percentage_change/100];
deltaR=(R_range(2)-R_range(1))/length(Rin(:,1));
Rin(:,2)=R_range(1):deltaR:R_range(2)-deltaR;

out=sim(model_name)
```

```
out =
  Simulink.SimulationOutput:

    ScopeData: [1x1 struct]
    logstdout: [1x1 Simulink.SimulationData.Dataset]
    simout: [1x1 timeseries]
    tout: [6006x1 double]


    SimulationMetadata: [1x1 Simulink.SimulationMetadata]
    ErrorMessage: [0x0 char]
```

```
temp_vin = out.simout.Data(:,1);
temp_vout = out.simout.Data(:,2);

% Plot results
figure

figure
plot(Rin(100:end,2)-R_nominal,temp_vout(100:end-1))
title('Linearized quarter bridge')
xlabel('\Delta R (\Omega)')
```
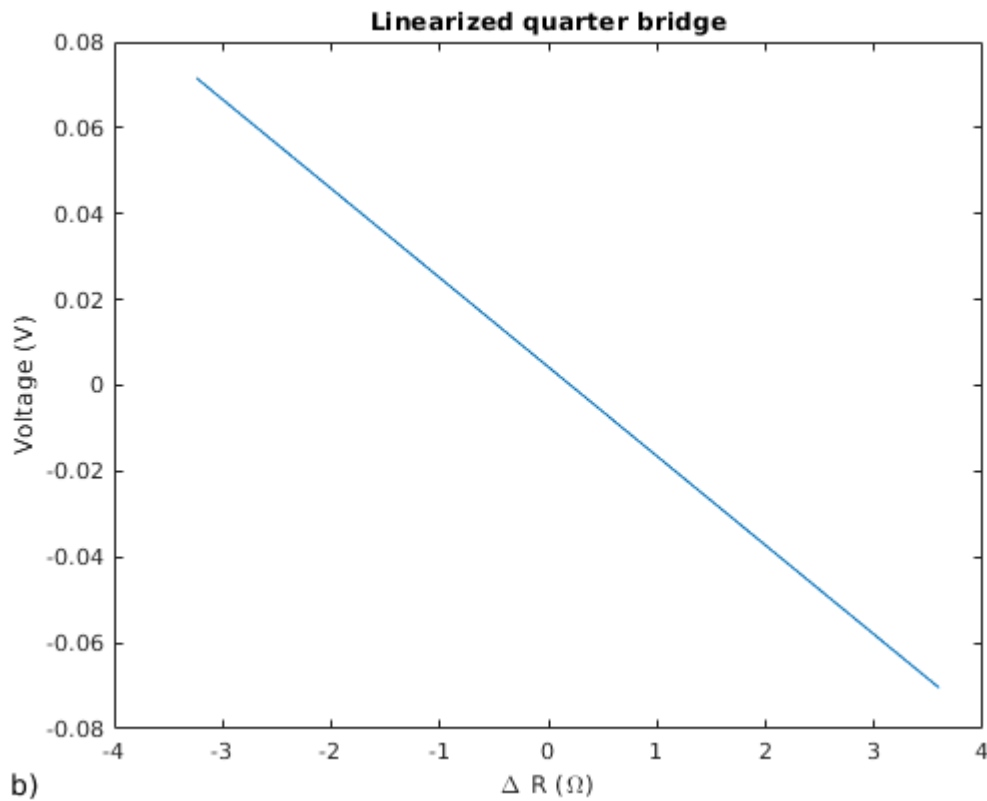
```
ylabel('Voltage (V)')  
annotation_save('b)', "Fig3.9b.jpg", SAVE_FLAG);
```



## Exersizes

Excercise 1: What is the Sensitivity of the quarter bridge if the sensitivity is computed as range of the output voltages/reference voltage?